

Carleton University

Elec4700 Assignment 4

Circuit Modeling



Name: Khaled AbouShaban





Student Number: 101042658



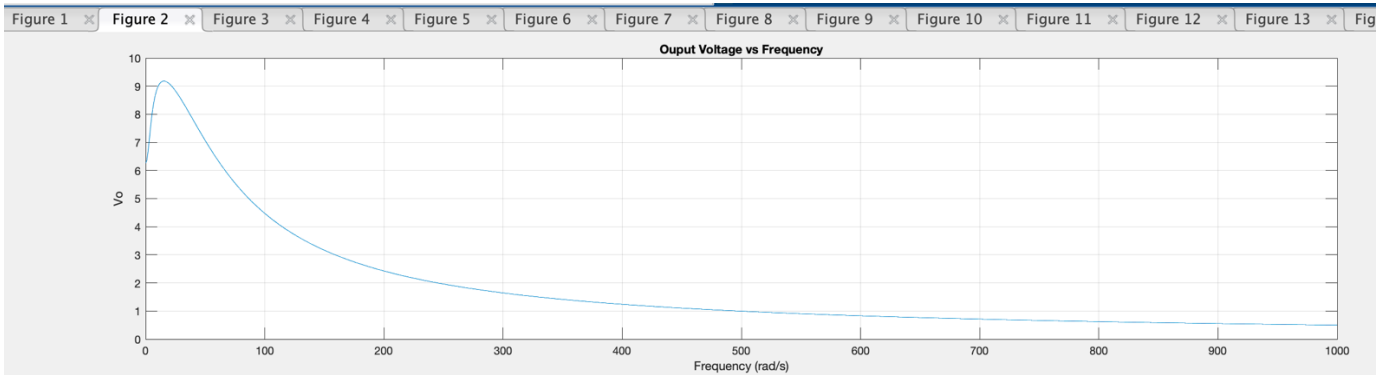
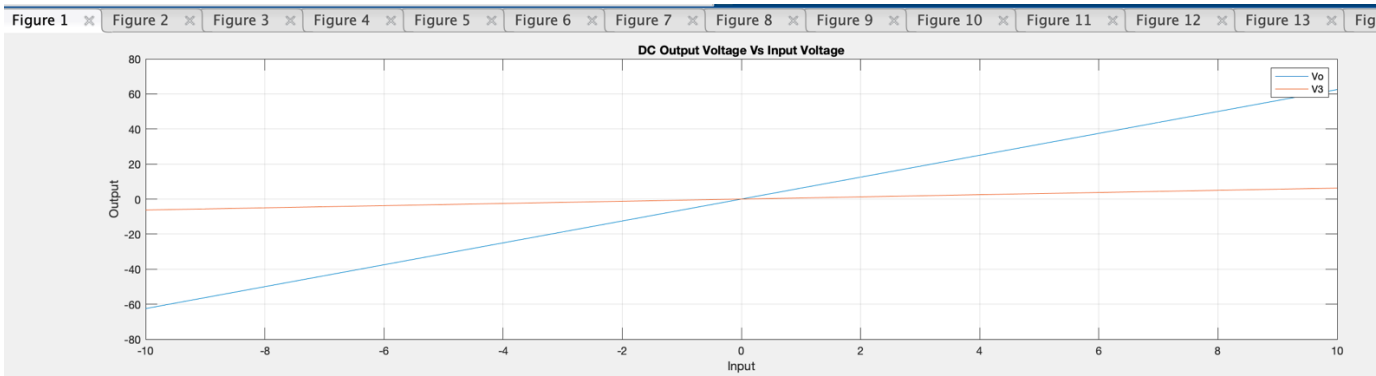
Part 1:

```
G =
    1.0000    0    0    0    0    0    0
   -1.0000    1.5000    0    0    0    1.0000    0
    0    0    0.1000    0    0   -1.0000    0
    0    0    0.1000    0    0    0   -1.0000
    0    0    0   -10.0000   10.0010    0    0
    0    1.0000   -1.0000    0    0    0    0
    0    0    0    1.0000    0    0   -100.0000

Cm =
    0    0    0    0    0    0    0
   -0.2500    0.2500    0    0    0    0    0
    0    0    0    0    0    0    0
    0    0    0    0    0    0    0
    0    0    0    0    0    0    0
    0    0    0    0    0   -0.2000    0
    0    0    0    0    0    0    0
```



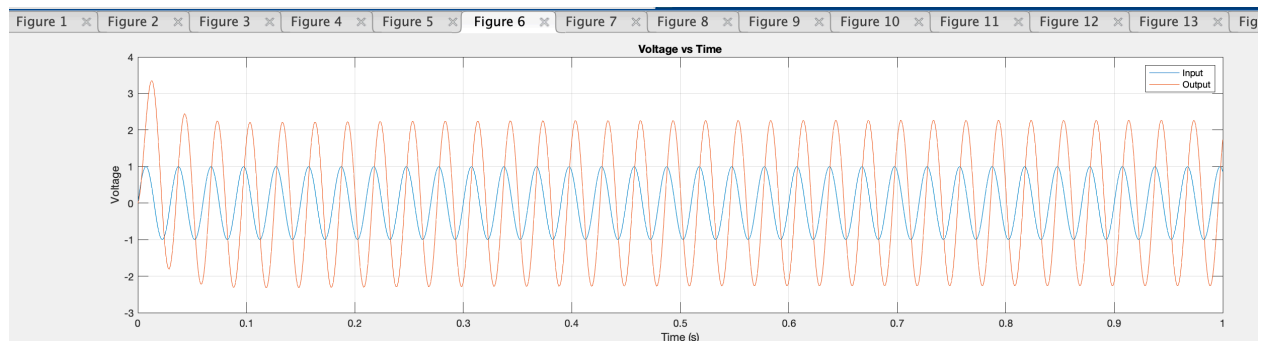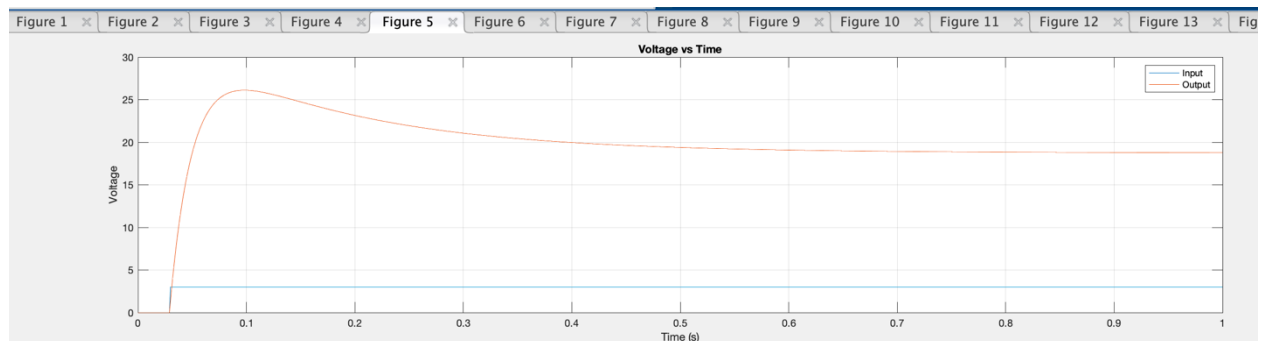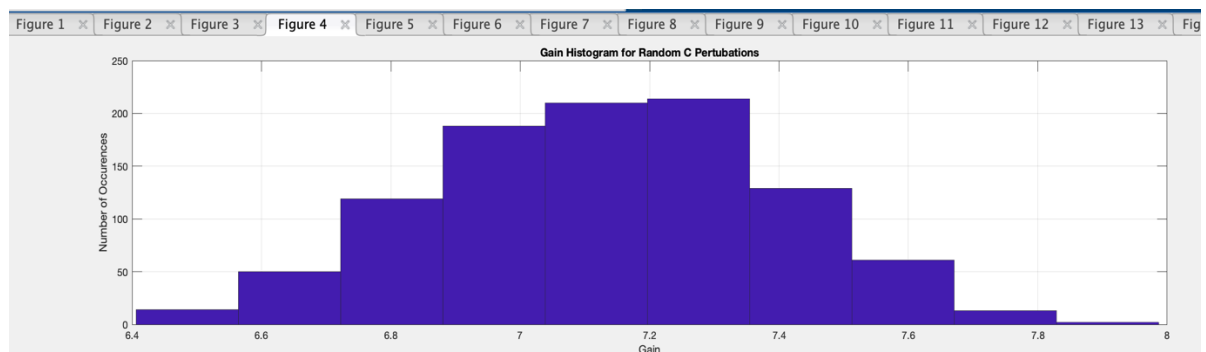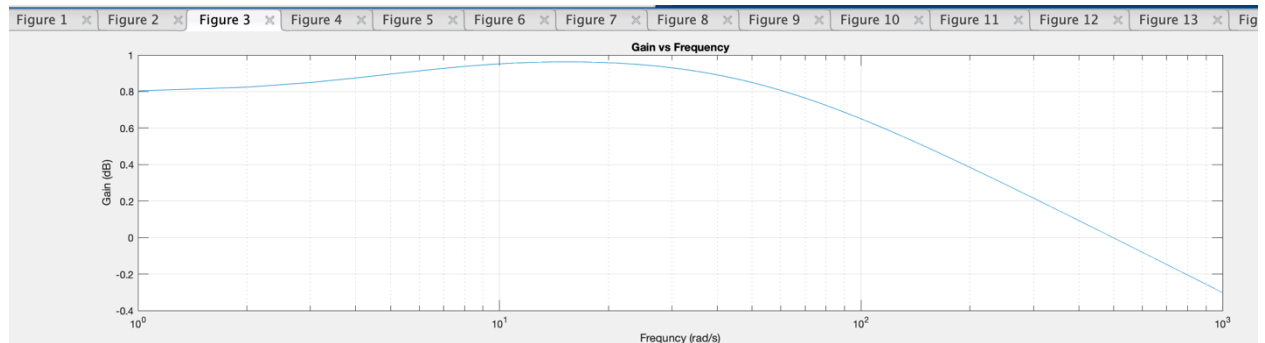

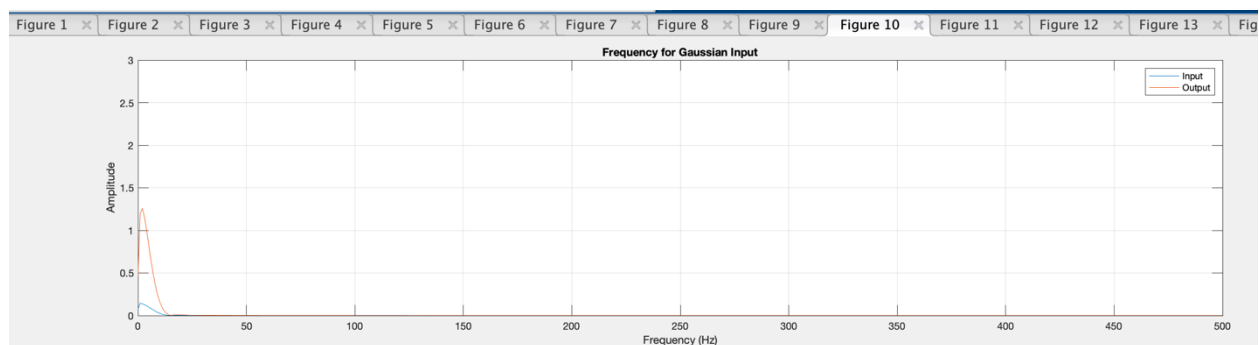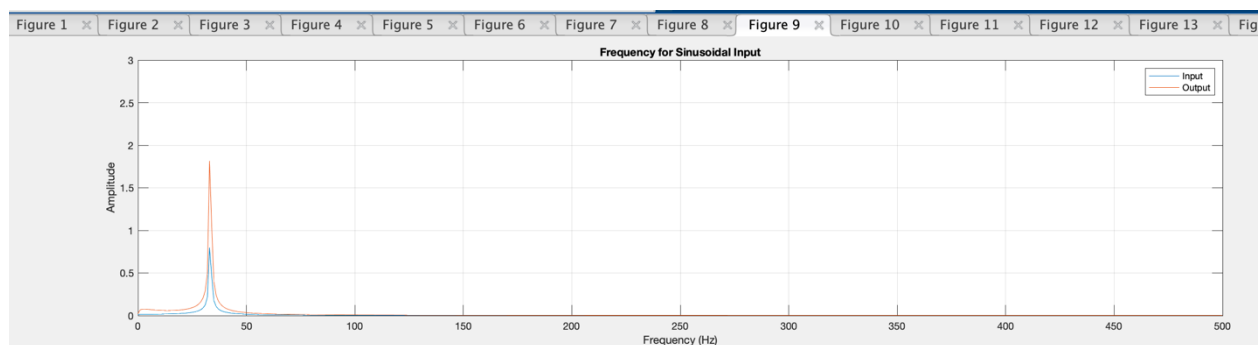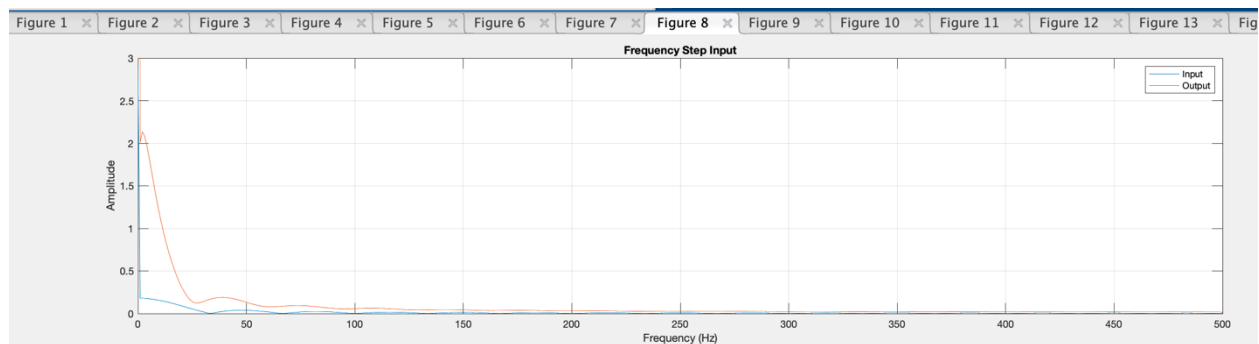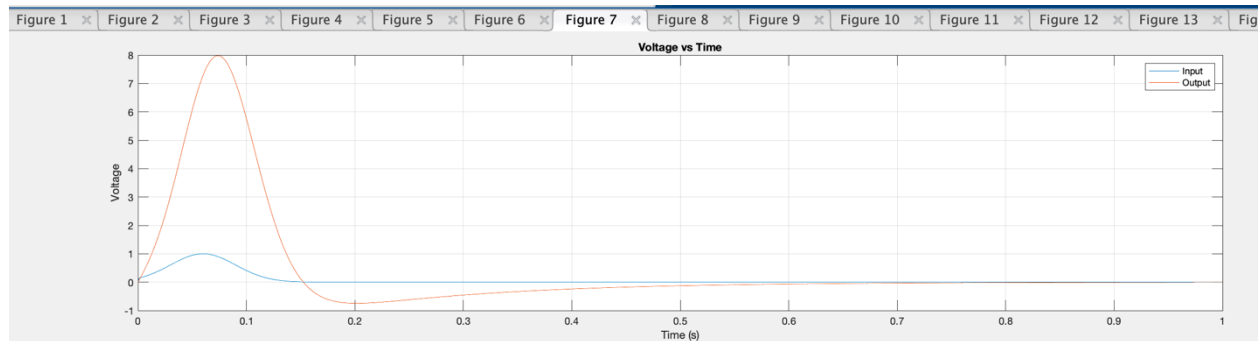



Circuit with Noise:





G =


1.0000	0	0	0	0	0	0
-1.0000	1.5000	0	0	0	1.0000	0
0	0	0.1000	0	0	-1.0000	0
0	0	0.1000	0	0	0	-1.0000
0	0	0	-10.0000	10.0010	0	0
0	1.0000	-1.0000	0	0	0	0
0	0	0	1.0000	0	0	-100.0000

Cm =

0	0	0	0	0	0	0
-0.2500	0.2500	0	0	0	0	0
0	0	0.0000	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	0	0
0	0	0	0	0	-0.2000	0
0	0	0	0	0	0	0

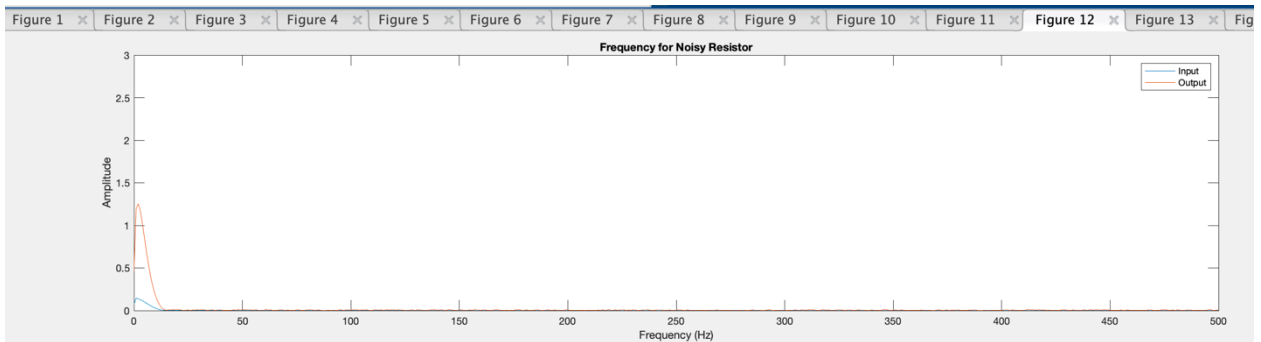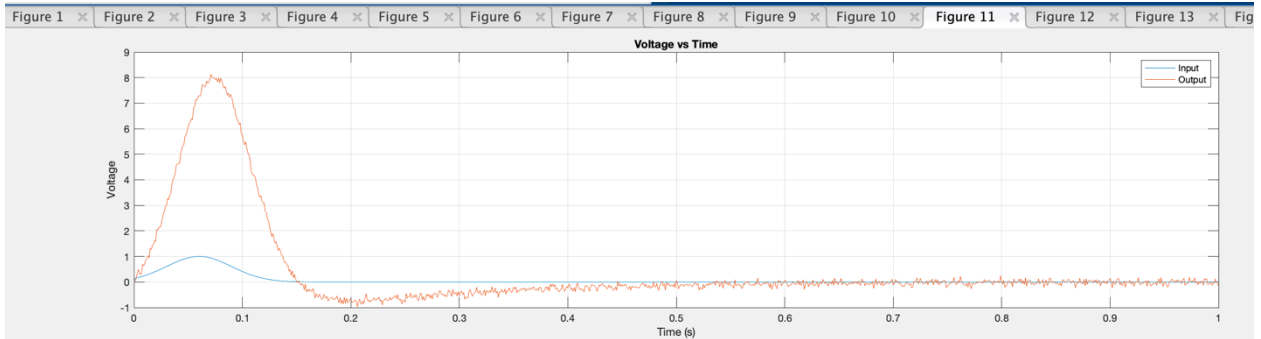

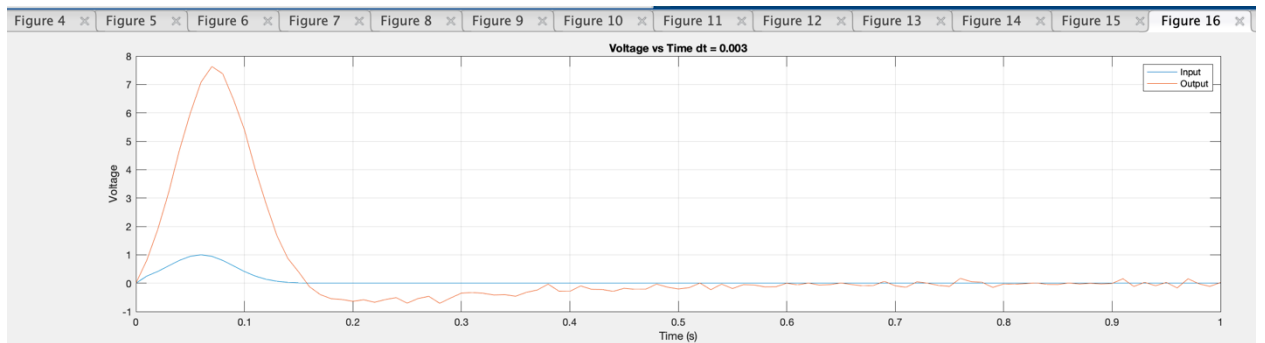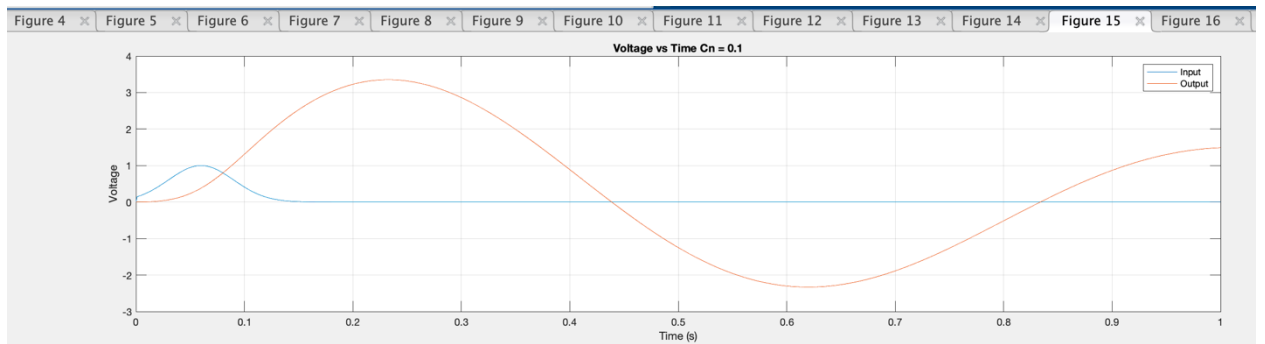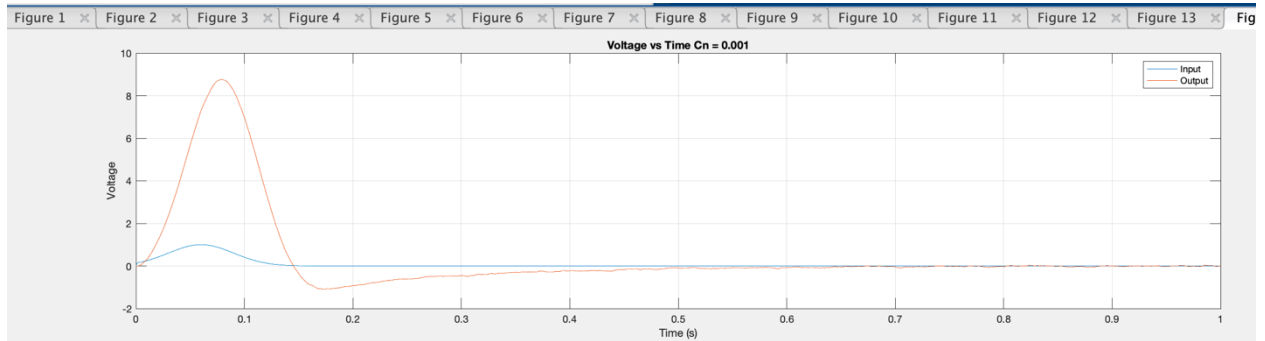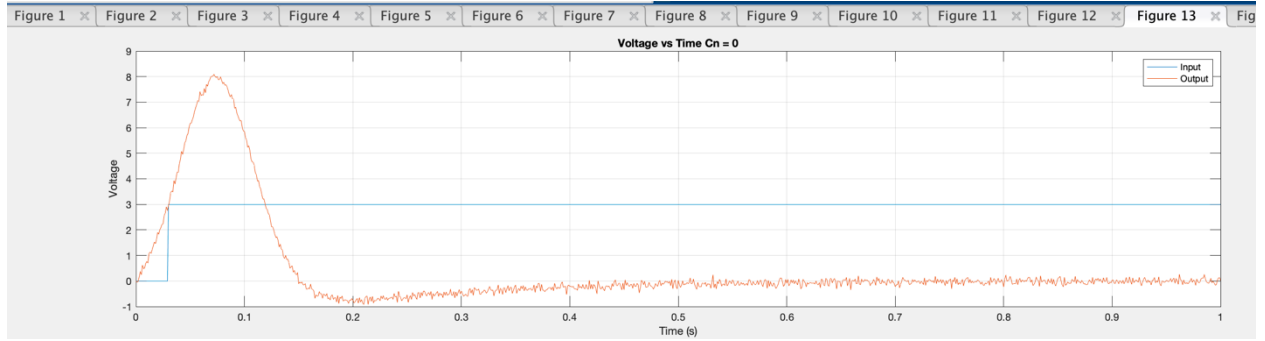

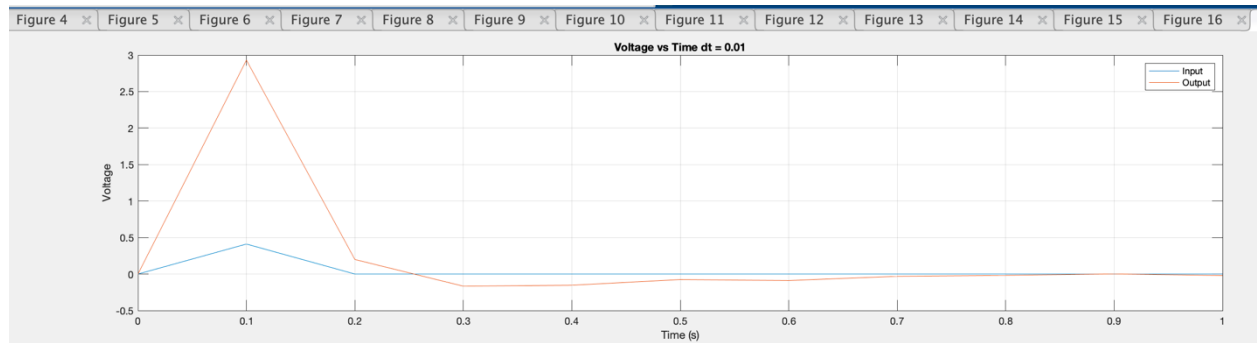

Non-Linearity:

If the circuit was modeled by the transconductance equation $V = \alpha I_3 + \beta I_3^2 + \gamma I_3^3$, The simulations would be altered to handle the non-linearity. A new column vector would be added, in order to deal with the non-linearity. The new vector would be added on the left of matrix equation such that a column B(V) and the system equation would change to the following:

$$V1 = V_in$$

$$G1(V2-V1) + C1 (d(V2-V1)/dt) + I1 = 0$$

$$G3V3 - I1 = 0$$

$$G3V3 - I3 = 0$$

$$G4(Vo-V4)GoVo = 0$$

$$V2 - V3 - L di/dt = 0$$

$$V4 - (\alpha I3 + \beta I3^2 + \gamma I3^3) = 0$$